

# INDUCTORLESS CHUA'S CIRCUIT

(based on <http://www.chuacircuits.com>)

The circuit shown below is a version of Chau's Circuit in which the physical inductor has been replaced by a synthesized inductor (aka: "gyrator") consisting of  $R_7$ ,  $R_8$ ,  $R_9$ ,  $R_{10}$ ,  $C$ , and two op-amps.

$L = (R_7 R_9 R_{10} C) / R_8$  for the synthesized inductor.

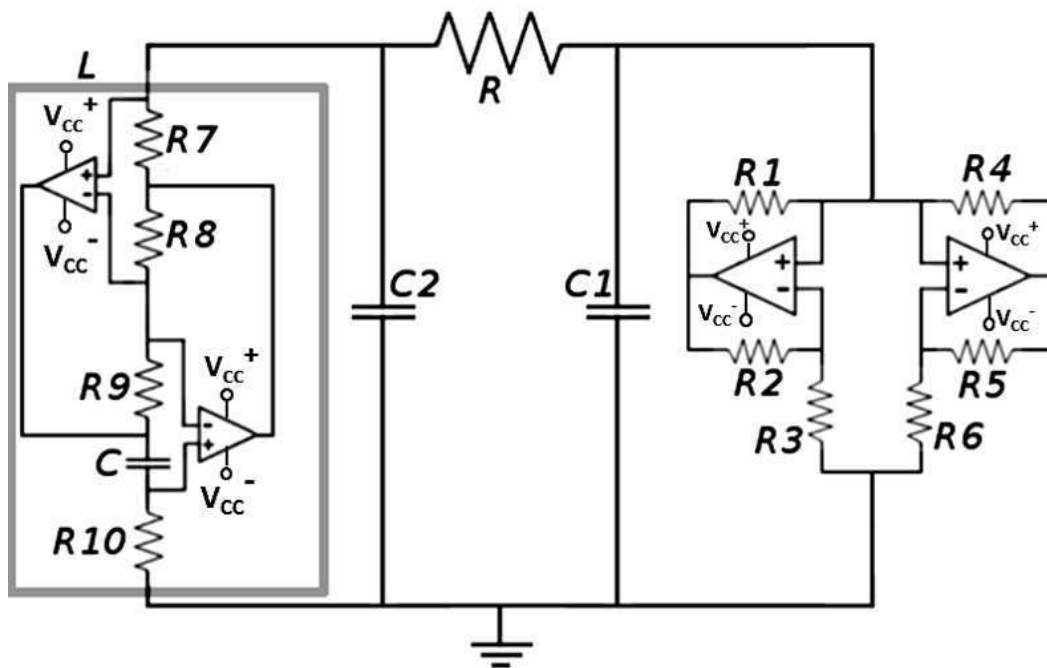


FIGURE A

## COMPONENTS

R=2.5 k $\Omega$ (pot.)	C=100 nF
R <sub>1</sub> =220 $\Omega$	C <sub>1</sub> =10 nF
R <sub>2</sub> =220 $\Omega$	C <sub>2</sub> =100 nF
R <sub>3</sub> =2.2 k $\Omega$	
R <sub>4</sub> =22.0 k $\Omega$	
R <sub>5</sub> =22.0 k $\Omega$	
R <sub>6</sub> =3.3 k $\Omega$	
R <sub>7</sub> =100 $\Omega$	
R <sub>8</sub> =1.0 k $\Omega$	
R <sub>9</sub> =1.0 k $\Omega$	
R <sub>10</sub> =2.5 k $\Omega$ (pot.)	

All op-amps are TL082 or equivalent.


Adjust R10 to a value of 1.8k Ohms to make the value of  $L = 18$  mH. (Alternatively, you can replace R10 with a 1.8k Ohm fixed resistor.)

There are 3 voltages that are important in this Inductorless Chua's circuit. These are shown in Figure B as X, Y, and P.

X is the voltage across the capacitor C<sub>1</sub>

Y is the voltage across the capacitor C<sub>2</sub>

P is the voltage at the junction of R7 and R8 (measured with respect to ground) which can be used to determine the current through the inductor,  $I_L$ , by the relation  $I_L = (V_P - Y)/R_7$

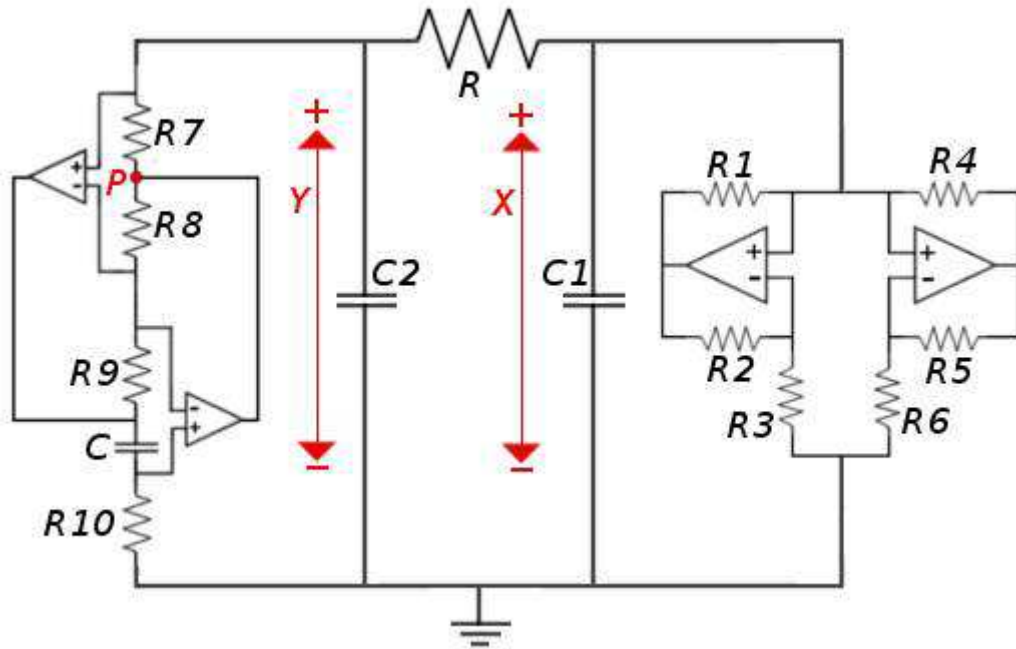

**FIGURE B**

**Take any two of the three voltages X, Y, and P. Display either one versus the other to get the strange attractor for this Inductorless Chau's Circuit.**